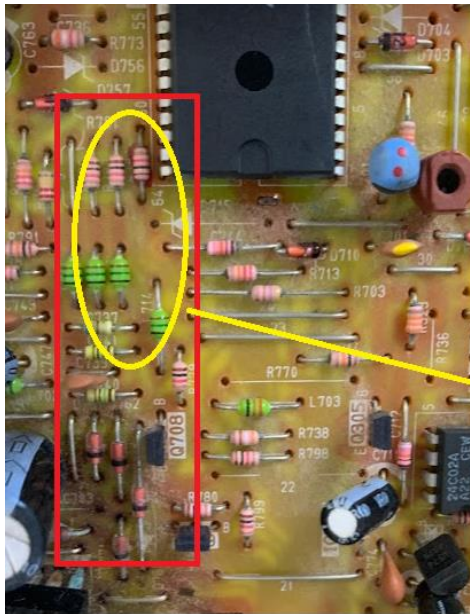



Mitsubishi CT29AX1

OSD:




**OSD**

**Two sets of resistors from RGB Lines**

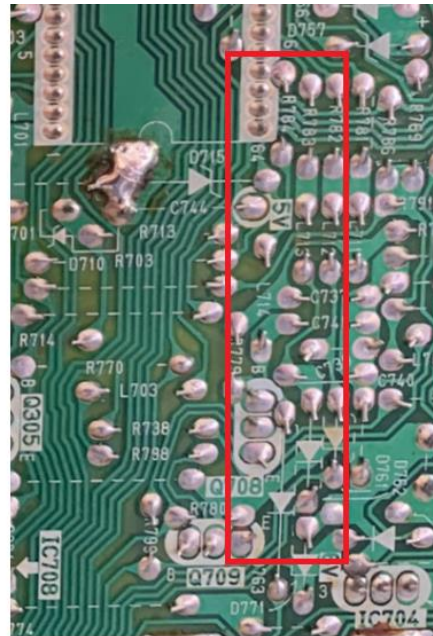

- I believe the brown resistors are 1k in value
- I don't know what the green ones are or for


Teletext Header:

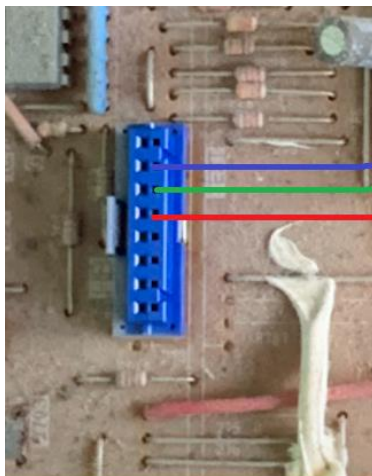

**I can now confirm these points have continuity with RGB pins on Jungle Chip**


- Teletext header inbetween OSD and Jungle chip , I can confirm lines have continuity with Jungle chip RGB pins.

Jungle Chip:

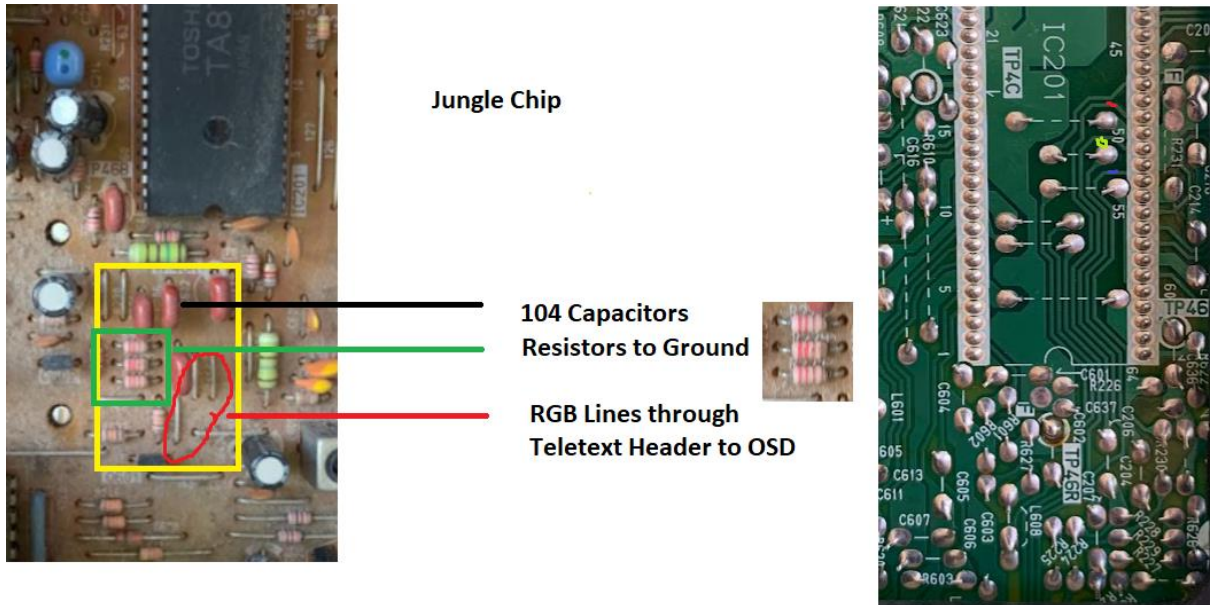

- 104 capacitors from Jungle chip RGB pins ,
- The resistors in green come off the 104 capacitors and are wired to ground , I am unsure what the value of these are or if these are the reason why I see now picture.

Current Breadboard setup:

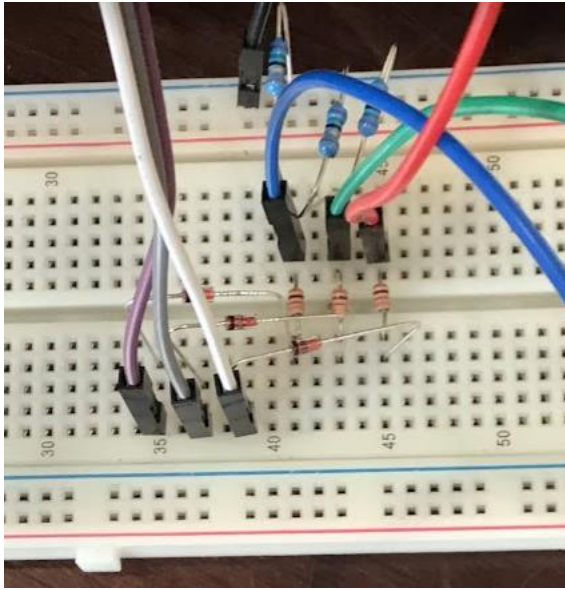

- RGB lines terminated to 75ohm resistors to ground , (Same ground as the rca ground connectors)
- I have tried combinations such as
  - No diodes
  - No teletext header resistors (I believe 1k)
  - Removed 75 resistors termination
- Each one of these combinations still does not result in a picture

How I See this in comparison to your Mux Method:

