

DIGITAL DESIGN COEN 212	Ted Obuchowicz/ Asim Al-Khalili	
Time Allowed: 3:00 hrs.	Dec 13, 2017	2 pages
Answer All Questions	No materials are allowed	

Question 1

- Design** a 3-8 decoder using NAND gates only. Mark the outputs with their corresponding binary values. (3 marks)
- Use a 3-8 decoder plus minimal extra logic gates to implement the following functions: (3 marks)
 - $F1(A,B,C) = \sum m(0,1,2)$
 - $F2(A,B,C) = \sum m(3,4,5)$
 - $F3(A,B,C) = \sum m(5,6,7)$
- Use a 4-1 MUX plus minimal extra logic gates to implement the following function: (4 marks)

$$F4(A,B,C,D) = A'B' + ABC' + AB'D$$

Question 2

- Design** a circuit that performs the following operations $Y = 5A$ where A is an unsigned 4 bit binary number $A_3A_2A_1A_0$. Give area and delay estimate of your design. [Assume all gates have equal area and delay. A full adder has 5 gates and a half adder has 2 gates]. (6 marks)
- What size of ROM is required to implement the above multiplier? (2 marks)

Question 3

Design a Decoder that receives a BCD number and displays a **L** or **S** on a 7-segment display as shown in Fig. 1 below. If a BCD number is greater than OR equal TO 5 then **L** is displayed, if the number is less than 5 then **S** should be displayed. Start with a truth table and derive final output in MINIMAL SOP form. Give final circuit diagram. (8 marks)

Fig. 1

