

Question 3) (10 Marks)

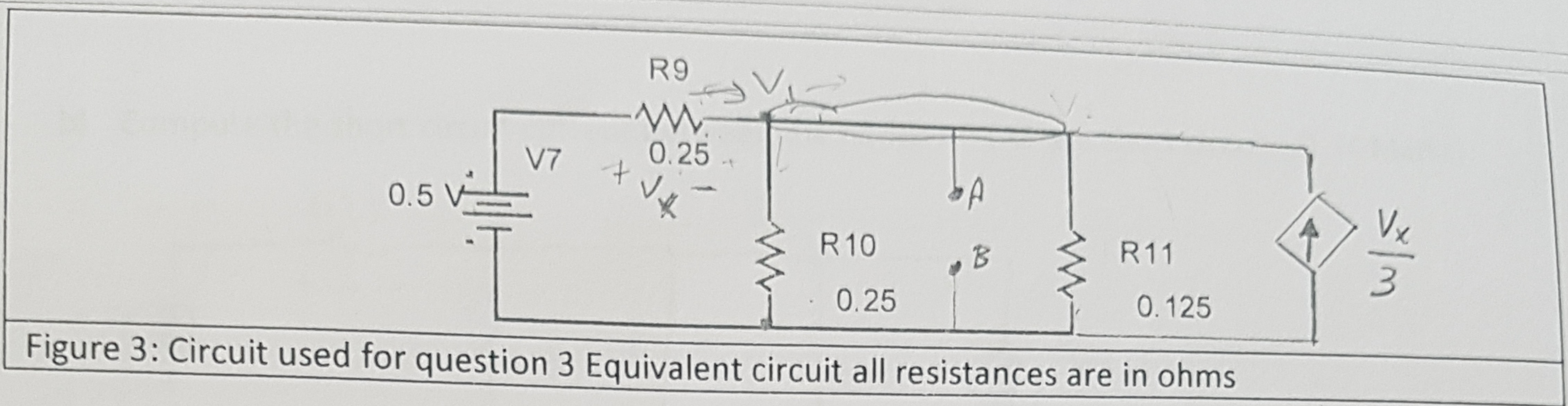


Figure 3: Circuit used for question 3 Equivalent circuit all resistances are in ohms

$$V_x = 0.5 - V_1$$

Use the circuit in figure 3 for this question.

- a) Compute the open circuit voltage between the nodes AB (AB are open circuited). (4 Marks)

Theremia:

$$\frac{V_1 - 0.5}{0.25} + \frac{V_1}{0.25} + \frac{V_1}{0.125} - \frac{0.5 + V_1}{3} = 0$$


$$12V_1 - 6 + 12V_1 + 24V_1 - 0.5 + V_1 = 0$$

$$49V_1 = 6.5 \quad \underline{V_1 = 0.133 \text{ V}} \rightarrow V_{th}$$

$$\underline{V_{AB} = 0.133 \text{ V}}$$


✓ 3

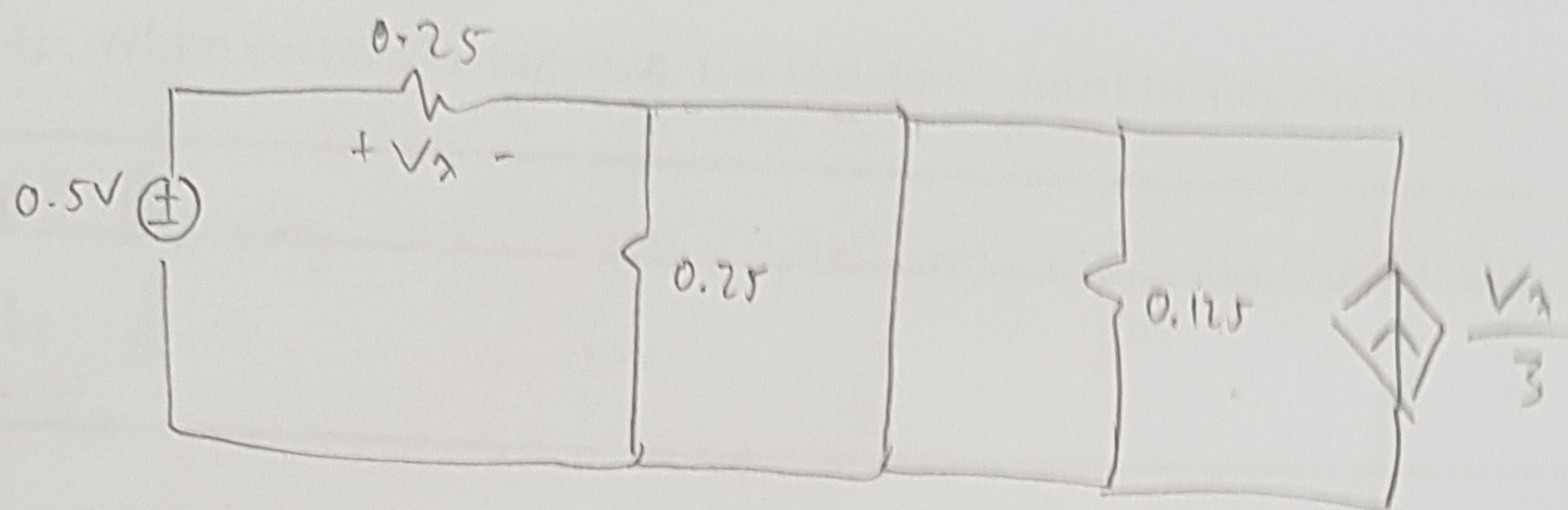b) Compute the short circuit current between the nodes AB (AB are short circuited). (4 Marks)



short circuit makes the resistances have 0 current

$$V_x = 0.5 = V_1$$

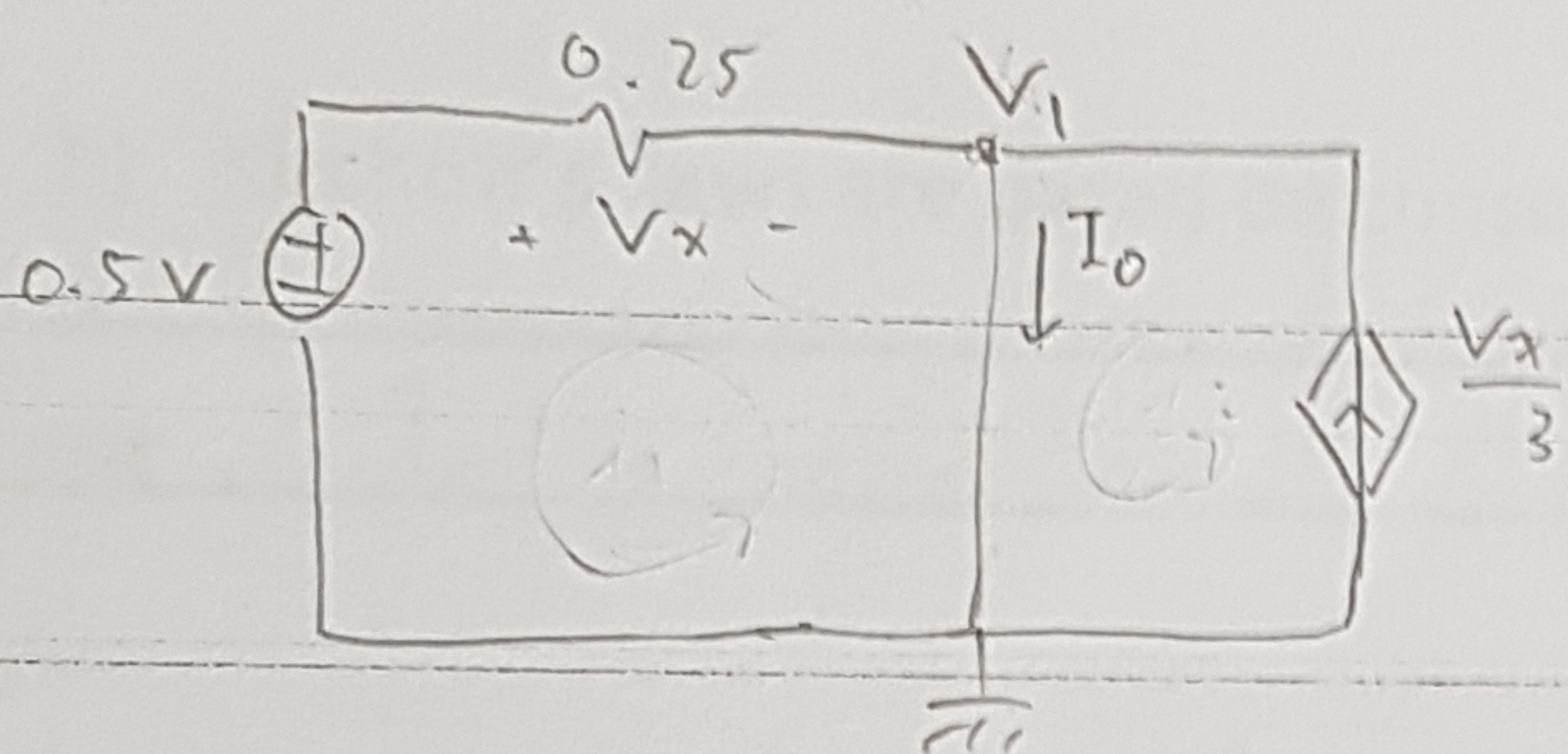

$$\frac{V_1 - 0.5}{0.25} - \frac{V_x}{3} = 0 \quad \text{+ } I_0$$

$$\frac{V_1 - 0.5}{0.25} - \frac{0.5 - V_1}{3} = 0$$

$$12V_1 - 6 - 0.5 - V_1 = 0$$

$$11V_1 = 6.5 \quad V_1 = 0.109 \text{ V}$$

$$V_x = 0.5 - 0.109 = 0.391 \text{ V}$$

$$I_0 = \frac{0.391}{3} + \frac{0.5}{0.25} \text{ A}$$

$$= 0.13 + 2 = \underline{2.13 \text{ A}}$$

$$I_0 = 2.13 \text{ A}$$

c) Compute the Thevenin equivalent resistance between the nodes AB: $R_{TH} = \frac{V_{OC}}{I_{SC}}$. (2 Marks)

$$R_{TH} = \frac{0.133}{2.13} = \underline{0.0624 \Omega}$$