

$$0 = (8 + j8)I_1 + (j2)I_2 - (j10)5 \Rightarrow$$

$$\Rightarrow (8 + j8)I_1 + (j2)I_2 = j50$$

$$-j20 = (j2)I_1 + (4 - j4)I_2 + (j2)5 \Rightarrow$$

$$\Rightarrow (j2)I_1 + (4 - j4)I_2 = -j30$$

$$0 = (-j10)I_1 + (j2)I_2 + (j8) \cdot 5 \Rightarrow$$

$$\Rightarrow (-j10)I_1 + (j2)I_2 = -j40$$

Page 1

ⓐ Loop 2

$$I_2 = \frac{-j30 - j2 I_1}{4 - j4}$$

ⓐ Loop 1

$$I_1 = \frac{j50 - j2 I_2}{8 + j8}$$

$$I_2 = \frac{-j30 - j2 \left( \frac{j50 - j2 I_2}{8 + j8} \right)}{4 - j4} \Rightarrow$$

$$\Rightarrow I_2 = \frac{-j30}{4 - j4} - \frac{j2 \left( \frac{j50 - j2 I_2}{8 + j8} \right)}{4 - j4} =$$



Page 8

$$I_2 = \left( \frac{15}{4} - j \frac{15}{4} \right) - j \frac{1}{32} (j 50 - j 2 I_2) =$$
$$= \left( \frac{15}{4} - j \frac{15}{4} \right) + \frac{25}{16} + \left( -\frac{1}{16} \right) I_2 \Rightarrow$$


$$\Rightarrow I_2 \left( 1 + \frac{1}{16} \right) = \frac{85}{16} - j \frac{15}{4} = 6,12 \angle -35,21^\circ$$

---

Page 3

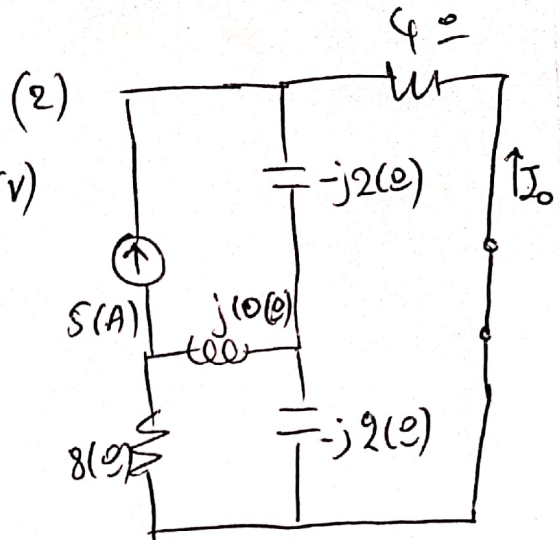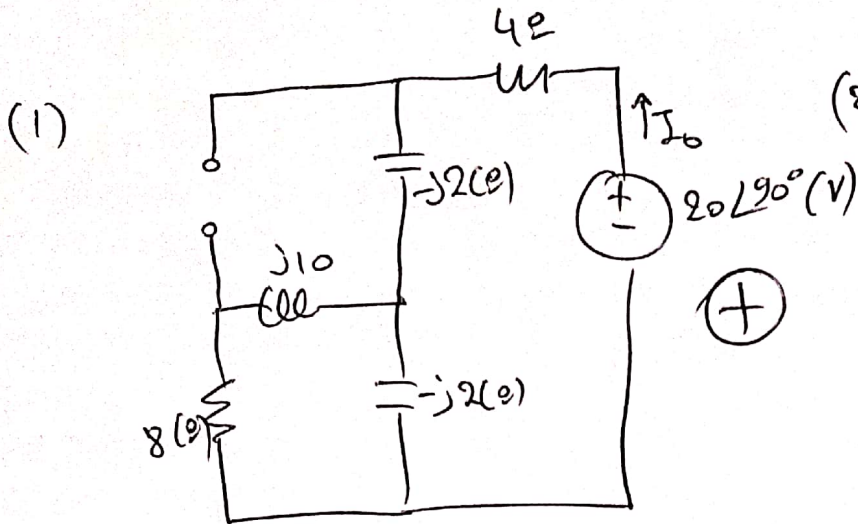

4.78  
OF

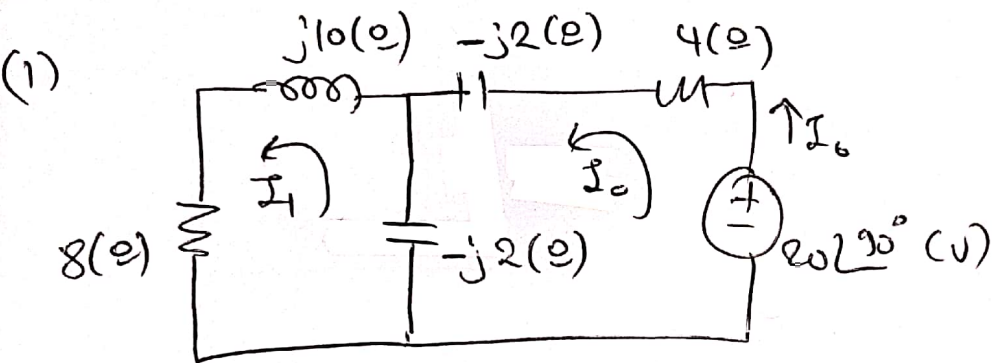

@ Loop 0 :  $j20 = (4 - j4) I_0 + j2(I_1)$

@ Loop 1 :  $0 = +j2 I_0 + (8 + j8) I_1$


$$I_0 = \frac{\begin{vmatrix} j20 & j2 \\ 0 & 8+j8 \end{vmatrix}}{\begin{vmatrix} 4-j4 & j2 \\ j2 & 8+j8 \end{vmatrix}} = \frac{(j20)(8+j8) - 0}{(4-j4)(8+j8) - (j2)(j2)} = \frac{-160 + j160}{64 - (-4)} =$$

$$= -\frac{40}{17} + j\frac{40}{17} \text{ (A)}$$

$$\left\{ 3.3275 \angle 135^\circ \text{ (A)} \right\}$$

Page 4

(2)

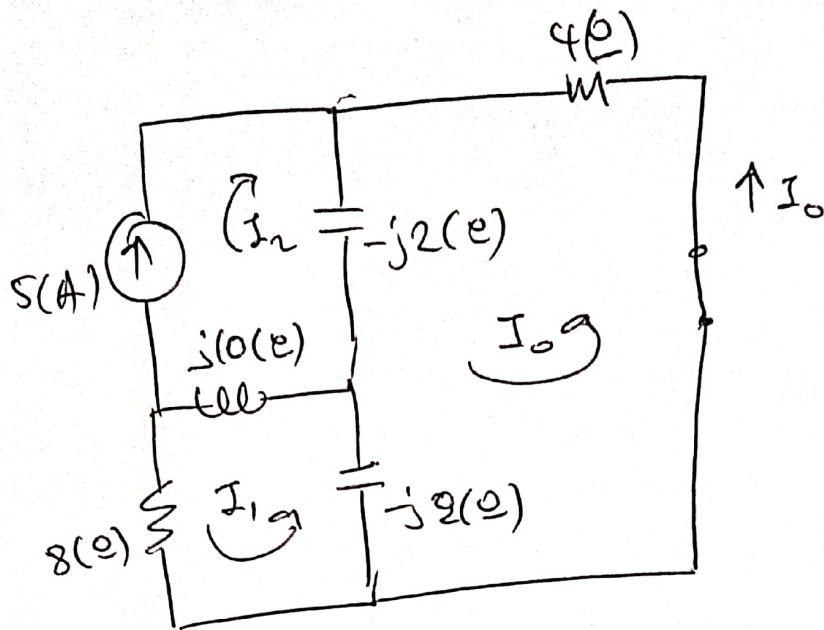

Loop 0 :  $0 = (4 - j4)I_0 + j2I_2 + (-j2)5 \Rightarrow$

$\Rightarrow +j10 = (4 - j4)I_0 + (j2)I_2$

Loop 1 :  $0 = (j2)I_0 + (8 + j8)I_1 + j10 \cdot 5 \Rightarrow$

$\Rightarrow -j50 = (j2)I_0 + (8 + j8)I_1$

Loop 2 :  $0 = (-j2)I_0 + j2I_1 + j8 \cdot 5 \Rightarrow$

$\Rightarrow (-j2)I_0 + (j2)I_1 = -j40$

$$\textcircled{a} \text{ Loop 0: } I_0 = \frac{j10 - j2 I_1}{4 - j4}$$

$$\textcircled{a} \text{ Loop 1: } I_1 = \frac{-j50 - j2 I_0}{8 + j8}$$

$$I_0 = \frac{j10 - j2 \left( \frac{-j50 - j2 I_0}{8 + j8} \right)}{4 - j4} =$$

$$= \frac{j10}{4 - j4} - \frac{j2}{(4 - j4)(8 + j8)} (-j50 - j2 I_0) =$$

$$= \frac{j10}{4 - j4} + \frac{j2 \cdot j50}{(4 - j4)(8 + j8)} + \frac{j2 j2}{(4 - j4)(8 + j8)} I_0 =$$

$$= -\frac{5}{4} + j\frac{5}{4} - \frac{25}{16} - \frac{1}{16} I_0 \Rightarrow$$

$$\Rightarrow I_0 \left( 1 + \frac{1}{16} \right) = -\frac{45}{16} + j\frac{5}{4} \Rightarrow I_0 = -\frac{45}{17} + j\frac{20}{17}$$

Page 6

$\left. \begin{matrix} 2,8967 \angle 156,037^\circ \\ (A) \end{matrix} \right\}$

$$I_0 = I_{0(1)} + I_{0(2)} = 6,12013 \frac{14478^\circ}{\text{or}} (A)$$

Page 7